

Fundamentals of Digital IC Design

Session2: Front End Design and Verification

Aug-2025 | NinePlus IT

Research Engineer, Namhyun Cho



1. Design Flow

What is RTL Design

2. Dataflow Modeling

Lab1. 4-Bit Binary Full Adders With Fast Carry

3. Behavioral Modeling

Lab3. Stopwatch


4. Structural Modeling

Lab3. Stopwatch


Where are we?

Cadence® Digital Realization of the RTL-to-GDSII Flow:

Design Spec & Logic Design

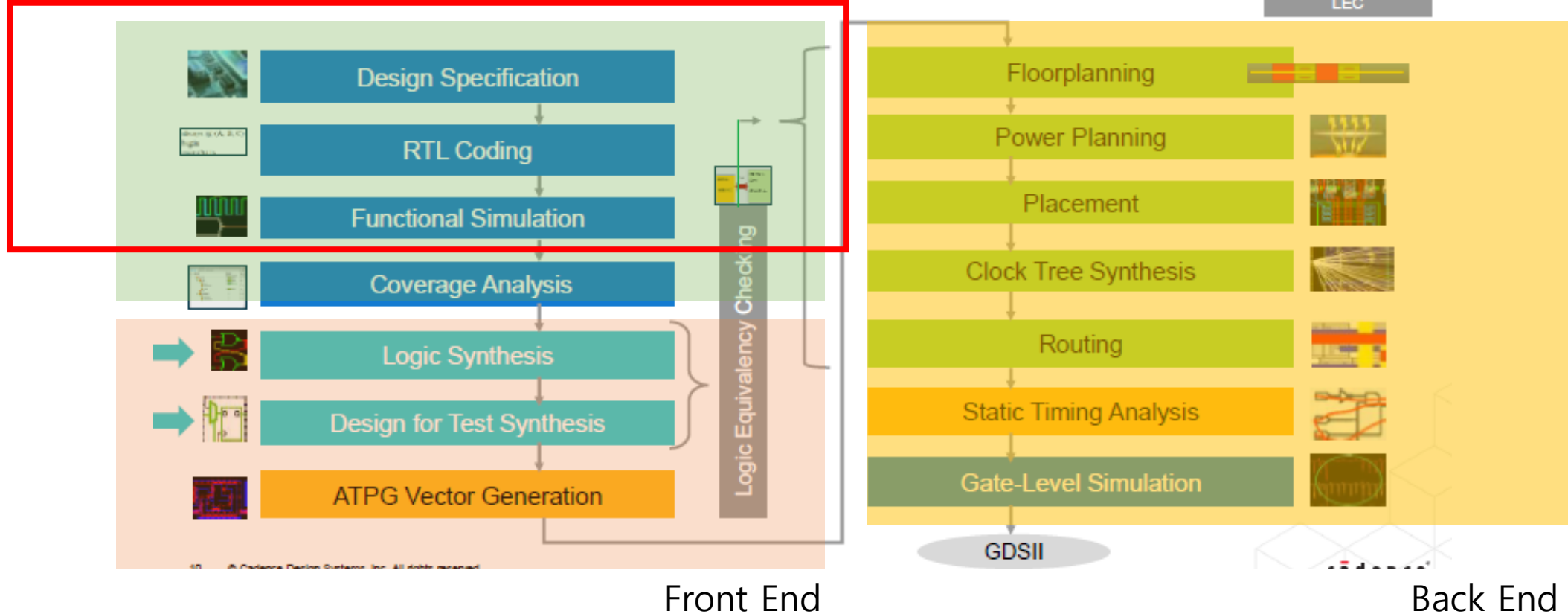

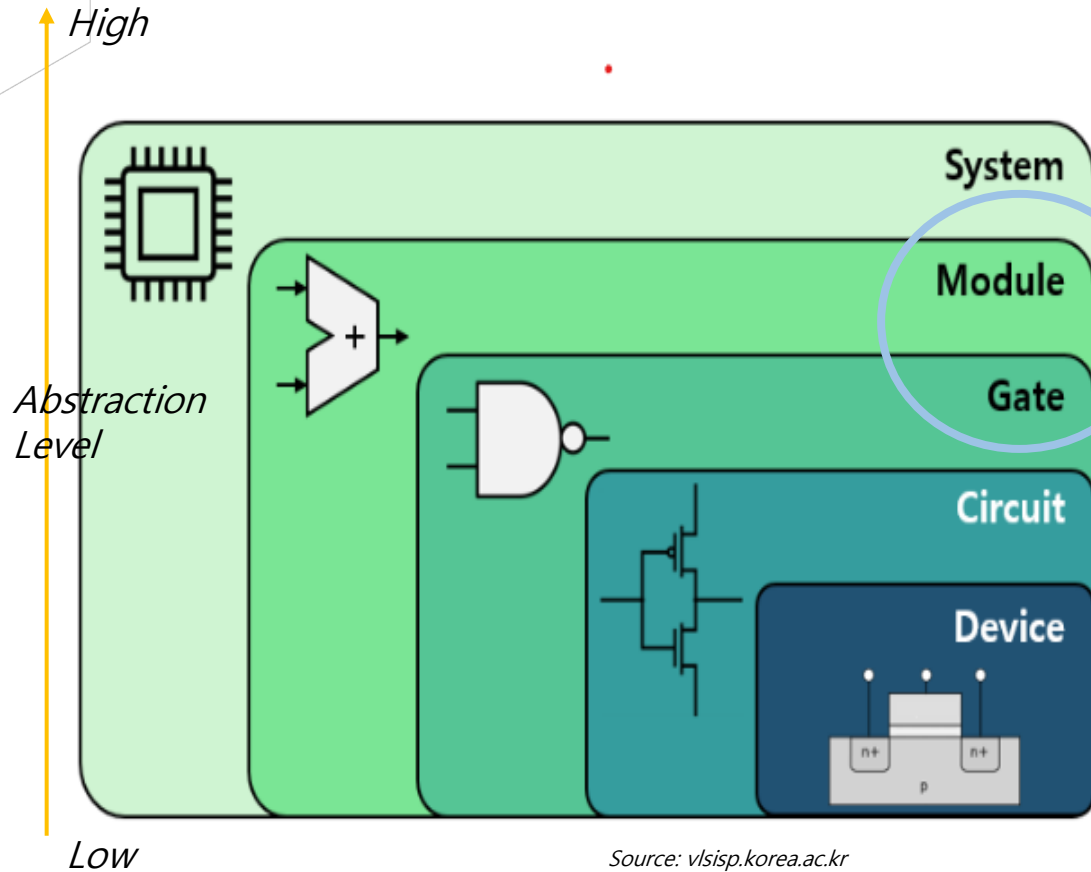Diverse viewpoint to scrutinize chip designs



Device Level

- 소자의 설계

Circuit Level

- TR기반의 회로설계

Gate Level

- Logic Gate기반의 회로설계



RTL(Module) Level

- 레지스터간 데이터 흐름 / 논리 연산 모델링 기반 회로설계


System Level

- 시스템 모듈 및 인터페이스를 통한 전체 시스템 설계


Semi-Custom IC Design

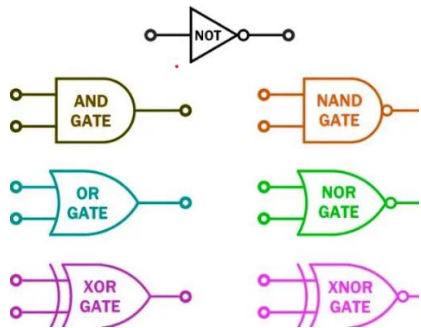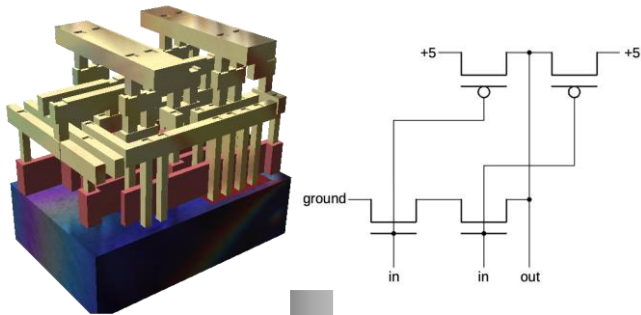

Standard Cell Library

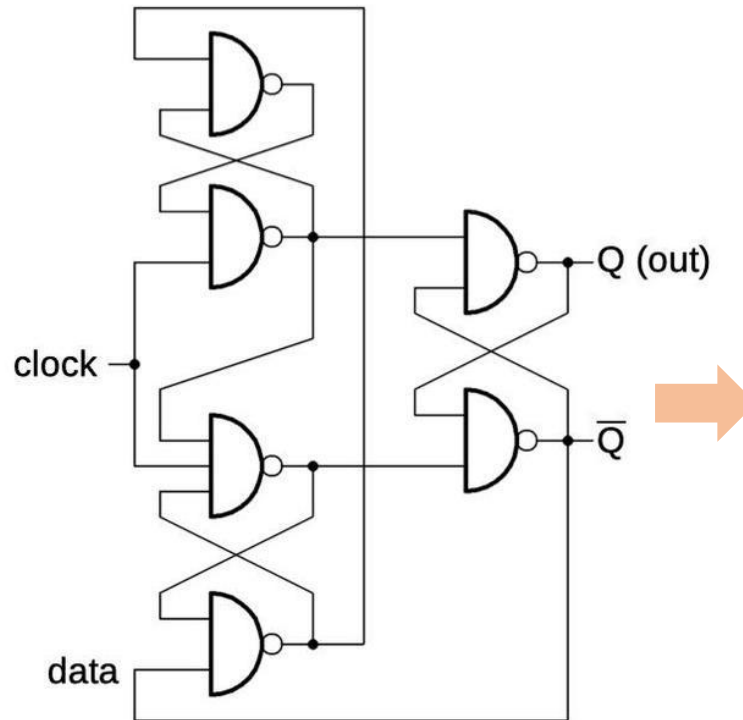

Logic HW Design

 

Implementation: Place & Route

FPGA (참고)

◆FPGA(Field Programmable Gate Array)

- ◆ Gate Level 수준에서 설계 진행
- ◆ Standard Cell이 미리 구현되어 있음 (LUT)


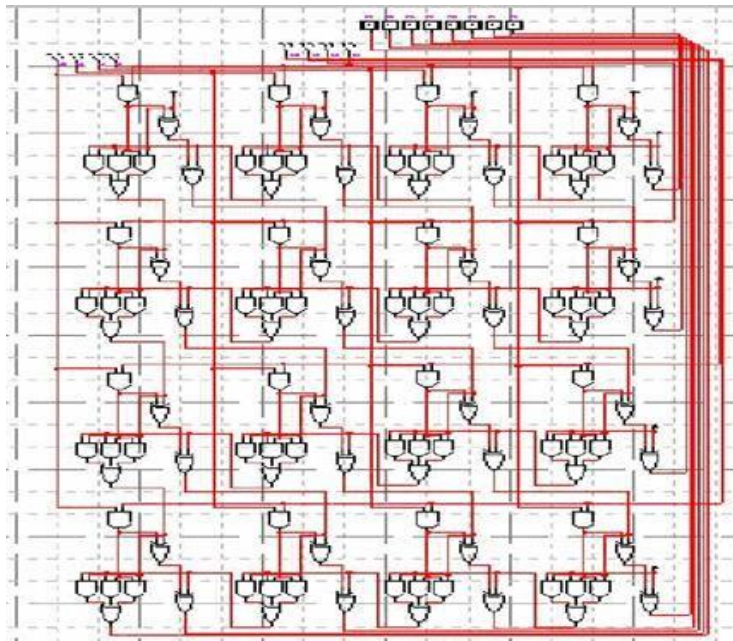


Fig. 4 X 4 multiplexer schematic

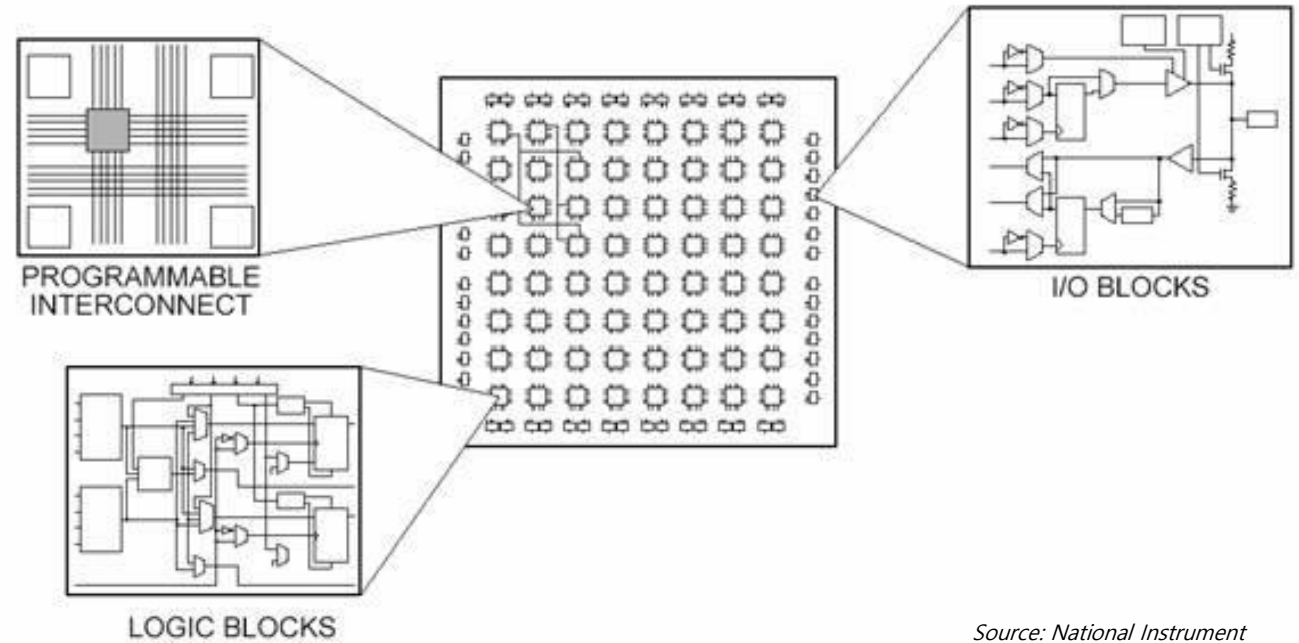

Source: National Instrument

Design Methodology

항목	DataFlow Modeling	Behavioral Modeling	Structural Modeling
기술 대상	데이터 흐름	동작 (제어 흐름)	게이트 / 모듈 연결 (인스턴스)
용도	간단한 조합 논리	FSM, 제어 로직 등	하드웨어 구조 묘사
추상화 수준	중간	높음	낮음

```

module mux2to1_dataflow (
    input wire A, B,
    input wire SEL,
    output wire Y
);
    assign Y = (SEL == 1'b0) ? A : B;
endmodule

```

```

module mux2to1_behavioral (
    input wire A, B,
    input wire SEL,
    output reg Y
);
    always @(*) begin
        if (SEL == 1'b0)
            Y = A;
        else
            Y = B;
        end
endmodule

```

```

module mux2to1_structural (
    input wire A, B,
    input wire SEL,
    output wire Y
);
    wire nSEL, outA, outB;


    not (nSEL, SEL);
    and (outA, A, nSEL);
    and (outB, B, SEL);
    or (Y, outA, outB);
endmodule

```



 1. Dataflow Modeling

Lab1. 4-Bit Binary Full Adders With Fast Carry



1. Specification

TYPES SN54283, SN54LS283, SN54S283, SN74283, SN74LS283, SN74S283
4-BIT BINARY FULL ADDERS WITH FAST CARRY
OCTOBER 1976—REVISED DECEMBER 1983

- Full-Carry Look-Ahead Across the Four Bits**
- Systems Achieve Partial Look-Ahead Performance with the Economy of Ripple Carry
- Supply Voltage and Ground on Corner Pins to Simplify P-C Board Layout

TYPICAL ADD TIMES

TYPE	TWO WORDS		TYPICAL POWER DISSIPATION PER ADDER
	8-BIT	16-BIT	
'283	23ns	43ns	310 mW
'LS283	25ns	45ns	95 mW
'S283	15ns	30ns	510 mW

description

The '283 and 'LS283 adders are electrically and functionally identical to the '83A and 'LS283, respectively; only the arrangement of the terminals has been changed. The 'S283 high performance versions are also functionally identical.

These improved full adders perform the addition of two 4-bit binary words. The sum (Σ) outputs are provided for each bit and the resultant carry (C4) is obtained from the fourth bit. These adders feature full internal look-ahead across all four bits generating the carry term in ten nanoseconds, typically, for the '283 and 'LS283, and 7.5 nanoseconds for the 'S283. This capability provides the system designer with partial look-ahead performance at the economy and reduced package count of a ripple-carry implementation.

The adder logic, including the carry, is implemented in its true form. End around carry can be accomplished without the need for logic or level inversion.

Series 54, Series 54LS, and Series 54S circuits are characterized for operation over the full temperature range of -55°C to 125°C. Series 74, Series 74LS, and Series 74S circuits are characterized for 0°C to 70°C operation.

SN54283, SN54LS283 ... J OR W PACKAGE
SN54S283 ... J PACKAGE
SN74283 ... J OR N PACKAGE
SN74LS283, SN74S283 ... D, J OR N PACKAGE

(TOP VIEW)

SN64LS283, SN54S283 ... FK PACKAGE
SN74LS283, SN74S283 ... FN PACKAGE

(TOP VIEW)

FUNCTION TABLE

INPUT				OUTPUT			
				WHEN C0 = L		WHEN C0 = H	
A1	B1	A2	B2	Σ1	Σ2	Σ3	Σ4
L	L	L	L	L	L	L	L
L	L	L	H	L	L	L	H
L	L	H	L	L	L	H	L
L	L	H	H	L	L	H	H
L	H	L	L	L	H	L	L
L	H	L	H	L	H	L	H
L	H	H	L	L	H	H	L
L	H	H	H	L	H	H	H
H	L	L	L	L	L	L	L
H	L	L	H	L	L	L	H
H	L	H	L	L	L	H	L
H	L	H	H	L	L	H	H
H	H	L	L	L	H	L	L
H	H	L	H	L	H	L	H
H	H	H	L	L	H	H	L
H	H	H	H	L	H	H	H

NOTE: Input conditions at A1, B1, A2, B2, and C0 are used to determine outputs Σ1 and Σ2 and the value of the internal carry C2. The values at C2, A3, B3, A4, and B4 are then used to determine outputs Σ3, Σ4, and C4.

TYPES SN54283, SN54LS283, SN54S283, SN74283, SN74LS283, SN74S283
4-BIT BINARY FULL ADDERS WITH FAST CARRY

logic diagram

Pin numbers shown on logic notation are for D, J or N packages.

schematics of inputs and outputs

'283

EQUIVALENT OF EACH INPUT

C0 input: $R_{eq} = 4 \text{ k}\Omega \text{ NOM}$
 Any A or B: $R_{eq} = 3.5 \text{ k}\Omega \text{ NOM}$

TYPICAL OF ALL OUTPUTS

C4 output: $R = 100 \Omega \text{ NOM}$
 Any Σ: $R = 120 \Omega \text{ NOM}$

'LS283

EQUIVALENT OF EACH INPUT

C0 input: $R_{eq} = 17 \text{ k}\Omega \text{ NOM}$
 Any A or B: $R_{eq} = 8.5 \text{ k}\Omega \text{ NOM}$

TYPICAL OF ALL OUTPUTS

100 Ω NOM

'S283

EQUIVALENT OF EACH INPUT

2.8 kΩ NOM

TYPICAL OF ALL OUTPUTS

50 Ω NOM

absolute maximum ratings over operating free-air temperature range (unless otherwise noted)

Supply voltage, V_{CC} (see Note 1)	7V
Input voltage: '283, 'S283	5.5V
'LS283	7V
Intermitter voltage (see Note 2)	5.5V
Operating free-air temperature range: SN54283, SN54LS283, SN54S283	-55°C to 125°C
SN74283, SN74LS283, SN74S283	0°C to 70°C
Storage temperature range	-65°C to 150°C

NOTES: 1. Voltage values, except intermitter voltage, are with respect to network ground terminal.
 2. This is the voltage between two emitters of a multiple-emitter transistor. This rating applies for the '283 and 'S283 only between the following pairs: A1 and B1, A2 and B2, A3 and B3, A4 and B4.

TEXAS INSTRUMENTS
 POST OFFICE BOX 228012 • DALLAS, TEXAS 75285

3-918

조합회로


- Gate-Level Modeling
- Data-Flow Modeling

Copyright © NineplusIT. All rights reserved.

The TTL Data Book Volume 2, Texas Instruments 9


What is the CLA?

< Ripple Carry Adder >

 


- 구조: 직렬구조
- 속도: 느림
- 면적: 작음

< Carry Lookahead Adder >

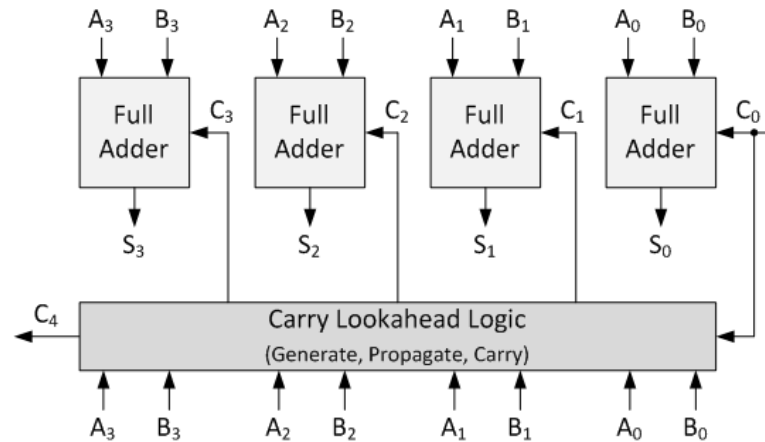

- 구조: 병렬계산
- 속도: 빠름
- 면적: 큰 편

< Kogge-Stone Adder >

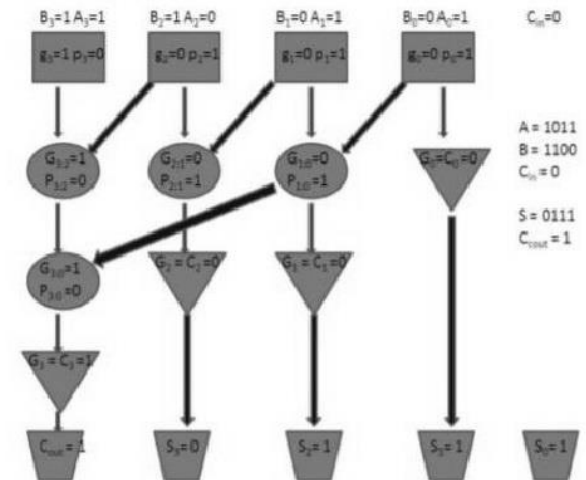

- 구조: 트리구조
- 속도: 매우 빠름
- 면적: 큼

What is the CLA?

< Ripple Carry Adder >

$$S_i = A_i \oplus B_i \oplus C_i$$

$$C_{i+1} = (A_i \cdot B_i) + (C_i \cdot (A_i \oplus B_i))$$

- 구조: 직렬구조
- 속도: 느림
- 면적: 작음

< Carry Lookahead Adder>

$$\text{Generate } (G_i): A_i \cdot B_i$$

$$\text{Propagate } (P_i): A_i \oplus B_i$$

$$C_{i+1} = G_i + (P_i \cdot C_i)$$

$$S_i = P_i \oplus C_i$$

- 구조: 병렬계산
- 속도: 빠름
- 면적: 큰 편

< Kogge-Stone Adder >

$$G_i = A_i \cdot B_i$$

$$P_i = A_i \oplus B_i$$


$$G_{i:j} = G_i + (P_i \cdot G_{j-1})$$

$$P_{i:j} = P_i \cdot P_{j-1}$$

$$C_{i+1} = G_{i:0}$$

- 구조: 트리구조
- 속도: 매우 빠름
- 면적: 큼

Port Declaration Principle

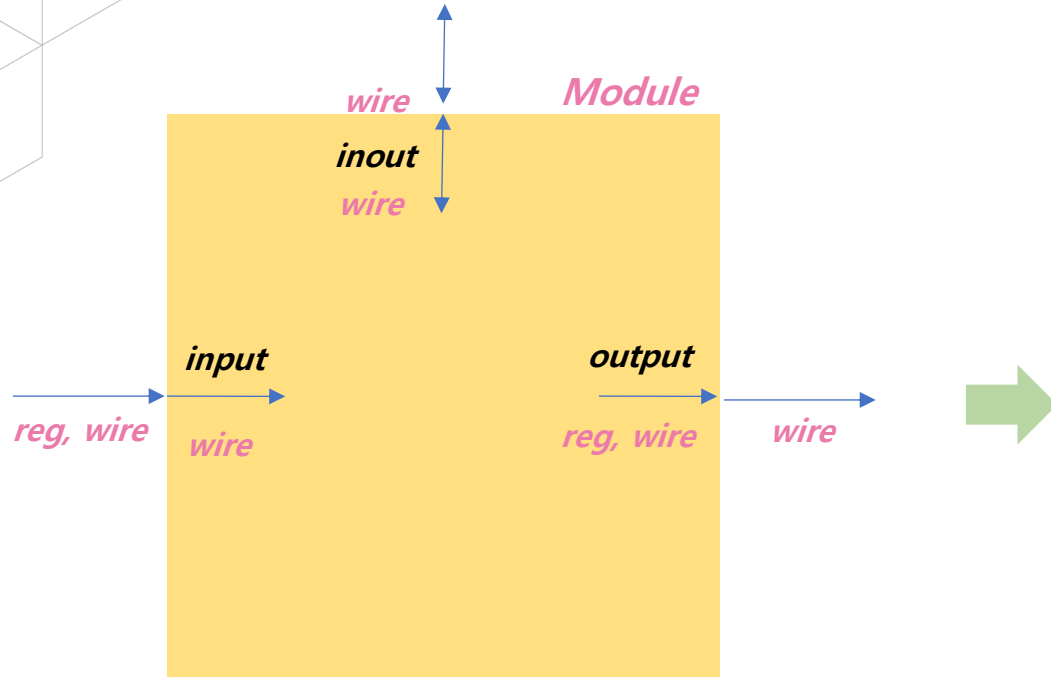

모듈을 기준으로,

1. input port는 wire
2. output port에 연결되는 신호는 wire
3. inout port는 wire, inout에 연결된 신호도 wire

- **wire**

- 다른 신호에 의해 지속적으로 구동
- 하드웨어 요소 또는 모듈 간의 연결

- **reg**

- 다른 값이 저장될 때까지 값을 유지

2. RTL Design

```
`timescale 1ns / 1ps
// SN74_283: 4-bit Binary Full Adder with Fast Carry

module SN74_283 (A, B, C0, S, C4);

    // Port declarations


    // Internal nets declarations

    // Internal signal Logic

    // Carry Lookahead Logic

    // Final Output Sum

endmodule
```

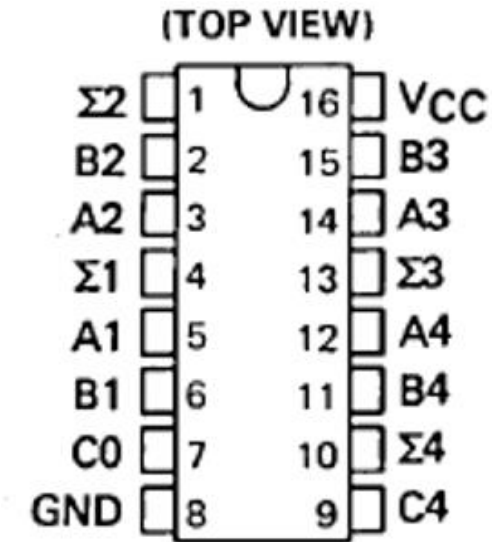

모듈과
포트 선언

포트의
입출력 정의
+
내부신호
정의

메인 로직
기술

Output
정의

3. Testbench

```
`timescale 1ns / 1ps
module tb_SN74_283();
// Port declarations
// DUT
// stimulus
endmodule
```


Delay	A	B	C0	C4	S
0	0000	0000	0	0	0000
10	0101	0011	0	0	1000
20	1111	0001	0	1	0000
30	1111	1111	1	1	1111
40	1010	0101	1	1	0000

➔ Test case는 많은 영역을 Cover 해야함 (Coverage)

1. 일반 동작 테스트
2. 특이점 테스트

실제로는, 설계자가 직접 모든 Case 기술할 수 없으므로
System-Verilog 기반으로 작성하거나, UVM Framework를 사용

4. Simulation

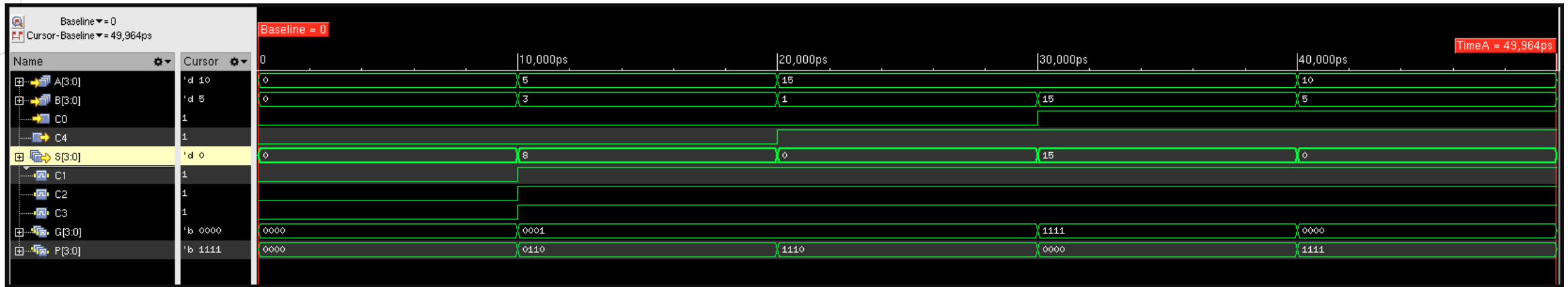


Delay	A	B	C0	C4	S
0	0000	0000	0	0	0000
10	0101	0011	0	0	1000
20	1111	0001	0	1	0000
30	1111	1111	1	1	1111
40	1010	0101	1	1	0000



2. Behavioral Modeling - FSM

Lab2. Traffic Signal Controller

 



0. Design Methodology

0. Design Methodology

```
`timescale 1ns / 1ps

module trafficsignal_fsm(clk, reset, i_ta, i_tb, o_sa, o_sb);
    // Port declaration

    // internal variable & parameter
    reg [1:0] state, next_state;

    // state parameter
    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b11;
    parameter S3 = 2'b10;

    // traffic light parameter
    parameter RED    = 2'b00;
    parameter YELLOW = 2'b01;
    parameter GREEN  = 2'b10;

    // status register
    always @(posedge clk or posedge reset) begin
        if (reset) state <= S0;
        else       state <= next_state;
    end

    // next state logic

    // output logic

endmodule
```


0. Design Methodology

```
`timescale 1ns / 1ps

module tb_traffic_signal_fsm();
    // Port declaration

    // internal parameter
    parameter clk_period = 10;

    // DUT

    // Reset sequence

    // Clock generation

    // Stimulus

endmodule
```




0. Design Methodology




3. Structural Modeling (No Gate-Level Modeling)


Lab3. Stopwatch

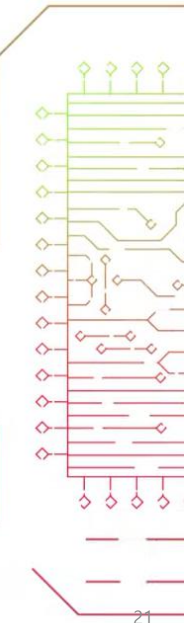

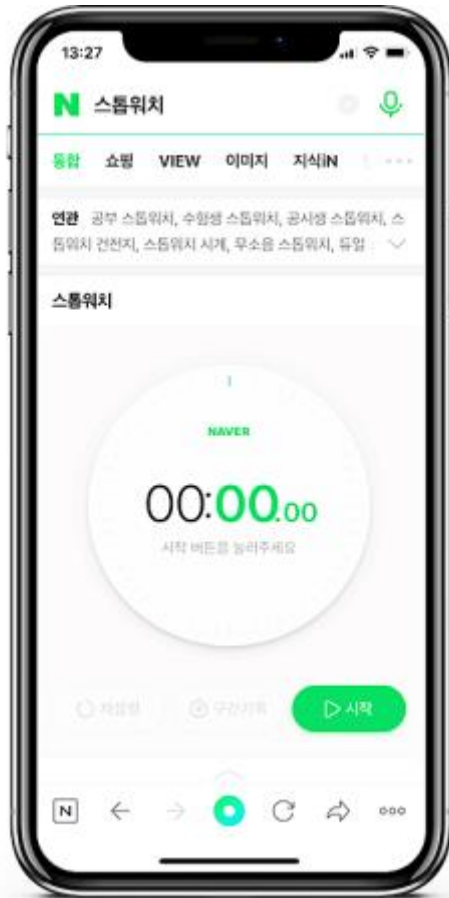1-1. Specification – Spec & State Diagram




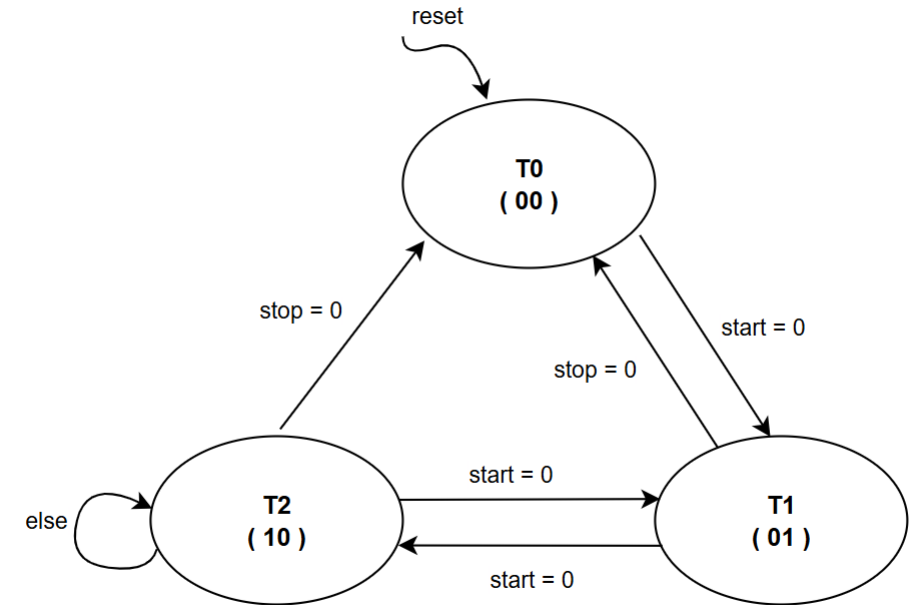- 시작: 시간 증가
- (증가하던 중에) 시작: 시간 일시정지
- (일시정지 중에) 시작: 시간 증가
- 정지: 0으로 초기화



< State Diagram >

1-2. Specification – Block Diagram

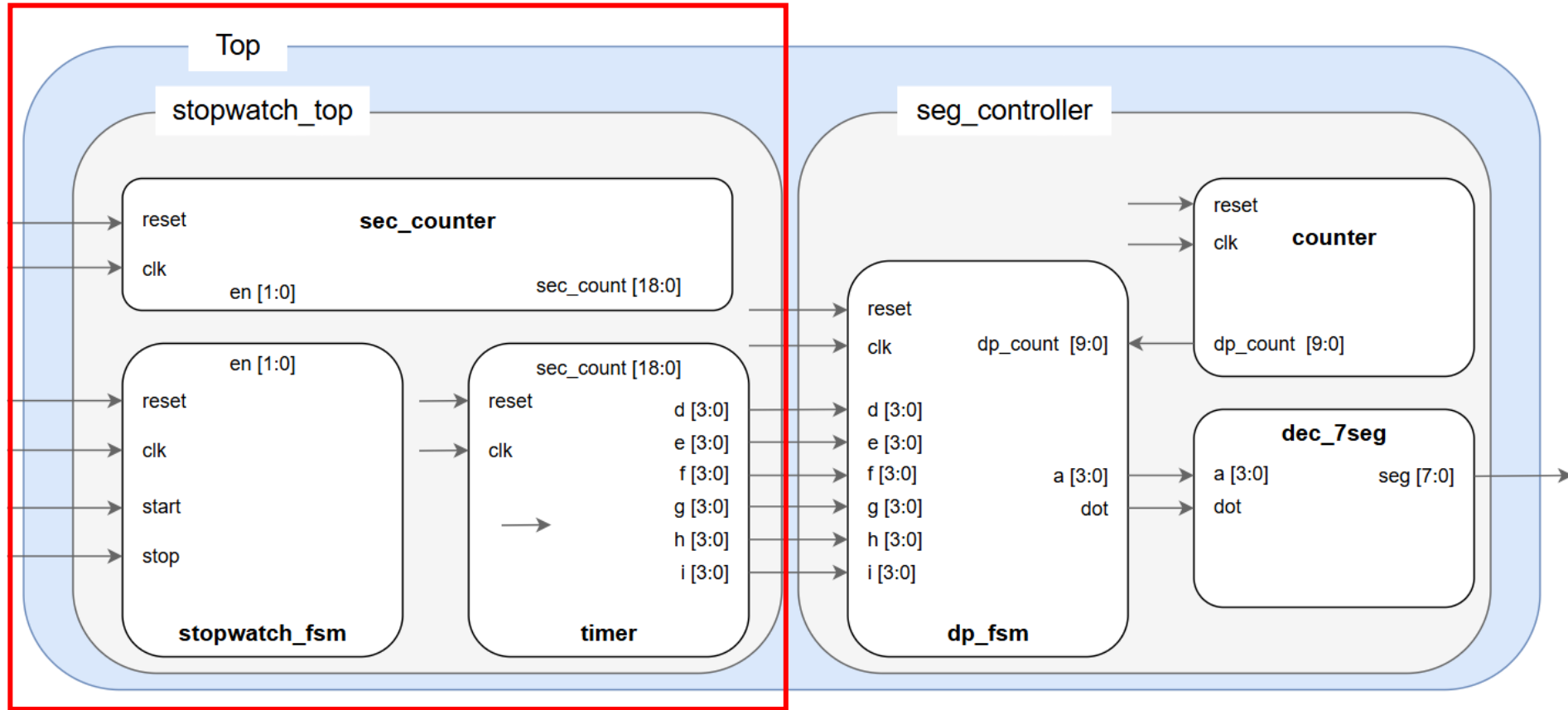

Our Target

Design Methodology

Top to Bottom Methodology



Bottom to Top Methodology

2. RTL Design

```

`timescale 1ns / 1ps
module sec_counter(clk, reset_n, en, sec_count);
    // port declaration
    // Logic
    // initialize counter at 10 clock cycle
endmodule

module timer(clk, reset_n, sec_count, stop, d, e, f, g, h, i);
    // port declaration
    // Logic
    // d~i, initialize g at 6
endmodule

module stopwatch_fsm(clk, reset_n, start, stop, en);
    //port declaration
    reg [1:0] state;
    reg [1:0] nextstate;


    parameter T0 = 2'b00; //base
    parameter T1 = 2'b01; //countup
    parameter T2 = 2'b10; //stop

    // state register
    always @(posedge clk or negedge reset_n) begin
        if (~reset_n) state <= T0;
        else state <= nextstate;
    end

    // next state logic
    // Output logic
endmodule

module stopwatch_top(clk, reset_n, start, stop, d, e, f, g, h, i);
    // port declaration
    // Instantiate
endmodule

```

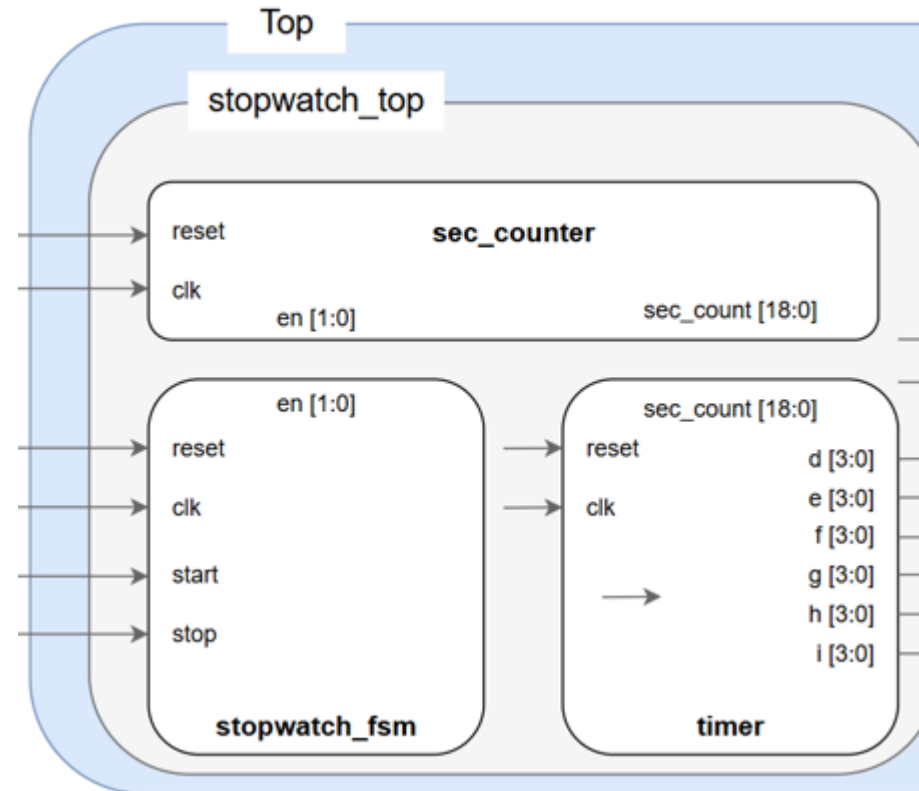

3. Testbench

```

`timescale 1ns / 1ps

module tb_stopwatch_top;

    // Port declaration

    // DUT

    // 50MHz Clock Generation (20ns period)

    // Task: press "start" for 1 clock cycle
    task press_start;
    begin

    end
    endtask

    // Task: press "stop" for 1 clock cycle
    task press_stop;
    begin

    end
    endtask

    // Stimulus
    initial begin
        // initialize

        // [1] Press start (T0 -> T1)

        // [2] Press start (T1 -> T2)

        // [3] Press start (T2 -> T1)

        // [4] Press stop (T0)

    end

    // Monitoring
    initial begin
        // dump waveform
        // dump variables
        // monitoring
    end
endmodule



```

```

xcelium> run
TIME      d  e  f  g  h  i  start  stop
   0:      0  0  0  0  0  0      1      1
   80:      0  0  0  0  0  0      0      1
  100:      0  0  0  0  0  0      1      1
  290:      1  0  0  0  0  0      1      1
  490:      2  0  0  0  0  0      1      1
  690:      3  0  0  0  0  0      1      1
  890:      4  0  0  0  0  0      1      1
 1090:      5  0  0  0  0  0      1      1
 1290:      6  0  0  0  0  0      1      1
 1490:      7  0  0  0  0  0      1      1
 1690:      8  0  0  0  0  0      1      1
 1890:      9  0  0  0  0  0      1      1
 2090:     10  0  0  0  0  0      1      1
 2100:     10  0  0  0  0  0      0      1
 2110:      0  1  0  0  0  0      0      1
 2120:      0  1  0  0  0  0      1      1
 4150:      0  1  0  0  0  0      0      1
 4170:      0  1  0  0  0  0      1      1
 4350:      1  1  0  0  0  0      1      1
 4550:      2  1  0  0  0  0      1      1
 4750:      3  1  0  0  0  0      1      1
 4950:      4  1  0  0  0  0      1      1
 5150:      5  1  0  0  0  0      1      1
 5350:      6  1  0  0  0  0      1      1
 5550:      7  1  0  0  0  0      1      1
 5750:      8  1  0  0  0  0      1      1
 5950:      9  1  0  0  0  0      1      1
 6150:     10  1  0  0  0  0      1      1
 6170:      0  2  0  0  0  0      1      1
 6350:      1  2  0  0  0  0      1      1
 6550:      2  2  0  0  0  0      1      1
 6750:      3  2  0  0  0  0      1      1



```

4. Simulation

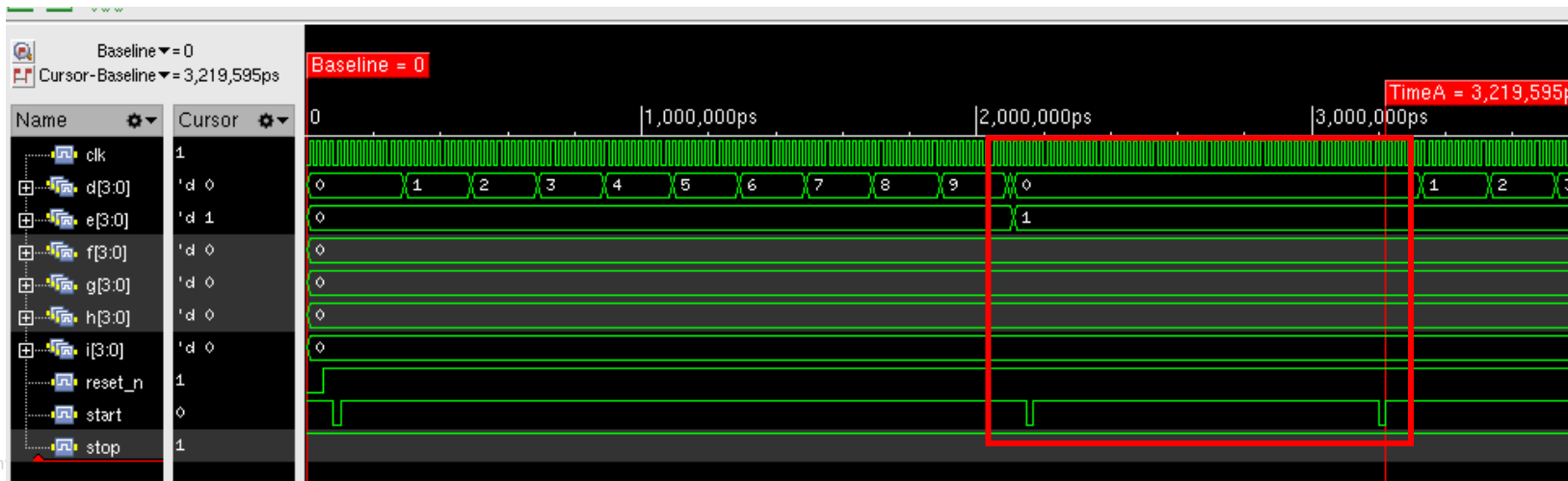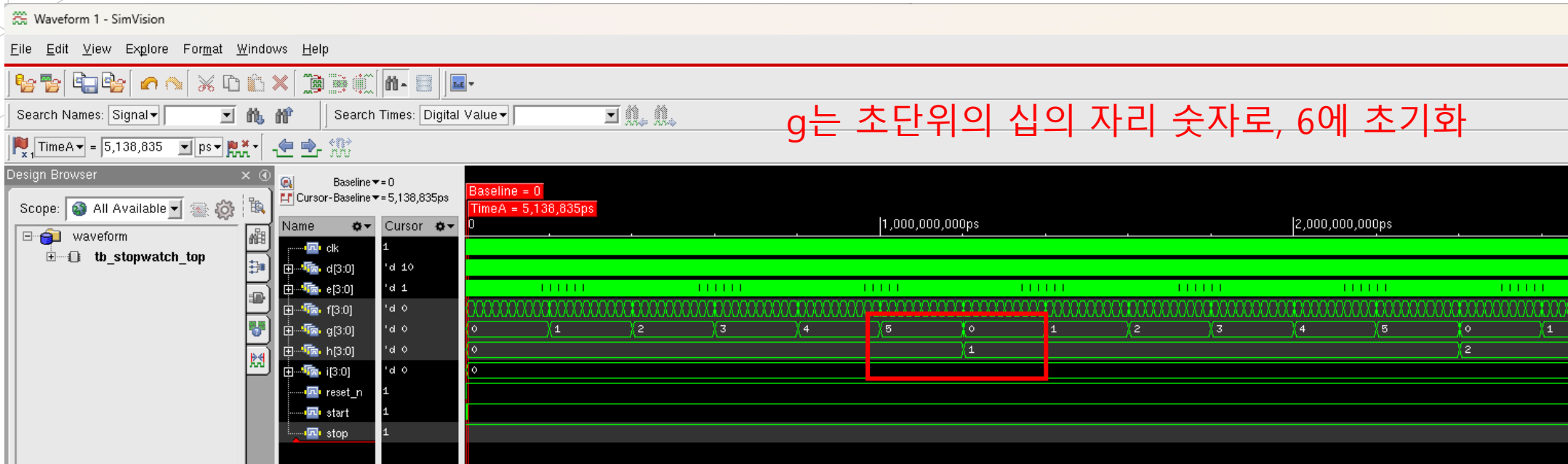

RTL 설계에서 Verilog Coding이 전부일까요?

Arithmetic Building Block - Adders

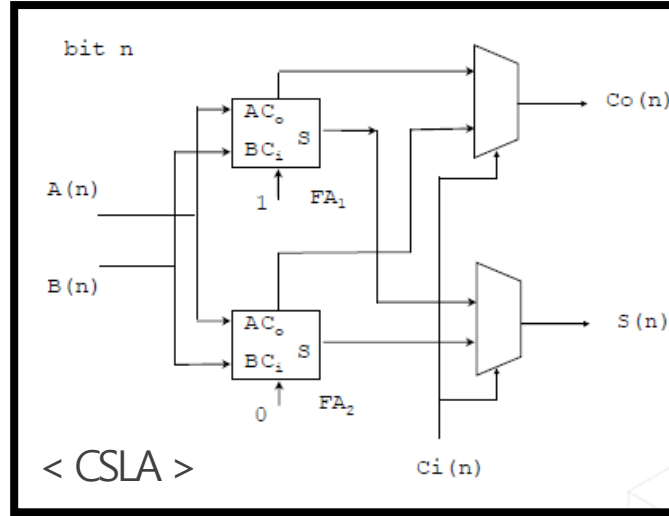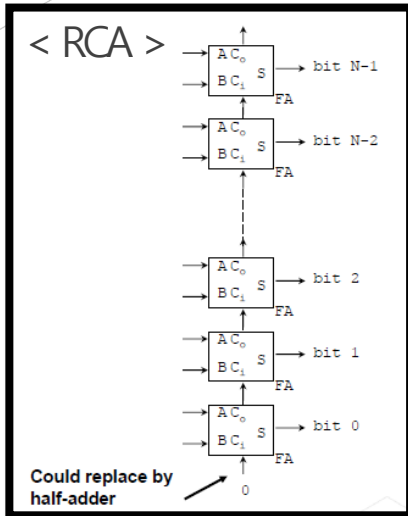

```
// Full Adder
module FA(output sum, cout, input a, b, cin);
    wire w0, w1, w2;

    xor (w0, a, b);
    xor (sum, w0, cin);

    and (w1, w0, cin);
    and (w2, a, b);
    or (cout, w1, w2);
endmodule

// Ripple Carry Adder - 8 bits
module RCA8(output [7:0] sum, output cout, input [7:0] a, b, input clk);
    wire [7:1] c;

    FA fa0(sum[0], c[1], a[0], b[0], 1'b0);
    FA fa[6:1](sum[6:1], c[7:2], a[6:1], b[6:1], c[6:1]);
    FA fa7(sum[7], cout, a[7], b[7], c[7]);
endmodule
```

```
// Full Adder
module FA(output sum, cout, input a, b, cin);
    wire w0, w1, w2;
    xor (w0, a, b);
    xor (sum, w0, cin);
    and (w1, w0, cin);
    and (w2, a, b);
    or (cout, w1, w2);
endmodule

// 4-bit Ripple Carry Adder
module RCA4(output [3:0] sum, output cout, input [3:0] a, b, input cin);
    wire [2:0] c;
    FA fa0(sum[0], c[0], a[0], b[0], cin);
    FA fa1(sum[1], c[1], a[1], b[1], c[0]);
    FA fa2(sum[2], c[2], a[2], b[2], c[1]);
    FA fa3(sum[3], cout, a[3], b[3], c[2]);
endmodule

// 1-bit 2:1 MUX
module MUX2to1_w1(output y, input i0, i1, s);
    assign y = s ? i1 : i0;
endmodule

// 4-bit 2:1 MUX
module MUX2to1_w4(output [3:0] y, input [3:0] i0, i1, input s);
    assign y = s ? i1 : i0;
endmodule

// 8-bit Carry Select Adder
module CSelA8(output [7:0] sum, output cout, input [7:0] a, b, input clk);
    wire [3:0] sum0, sum1, sum4_0, sum4_1;
    wire cout0_0, cout0_1, cout1_0, cout1_1;
    wire c1;

    RCA4 rca0_0(sum0, cout0_0, a[3:0], b[3:0], 1'b0);
    RCA4 rca0_1(sum1, cout0_1, a[3:0], b[3:0], 1'b1);
    MUX2to1_w4 mux0_sum(sum[3:0], sum0, sum1, 1'b0);
    MUX2to1_w1 mux0_cout(c1, cout0_0, cout0_1, 1'b0);

    RCA4 rca1_0(sum4_0, cout1_0, a[7:4], b[7:4], 1'b0);
    RCA4 rca1_1(sum4_1, cout1_1, a[7:4], b[7:4], 1'b1);
    MUX2to1_w4 mux1_sum(sum[7:4], sum4_0, sum4_1, c1);
    MUX2to1_w1 mux1_cout(cout, cout1_0, cout1_1, c1);
endmodule
```

Synthesis Report of Adders

< RCA >

```

Path 1: MET (3243 ps) Late Ext
  Group: clk
  Startpoint: (R) b[1]
  Clock: (R) clk
  Endpoint: (R) sum[7]
  Clock: (R) clk

  Capture
  Clock Edge:+ 10000
  Drv Adjust:+ 0
  Src Latency:+ 0
  Net Latency:+ 0 (
  Arrival:= 10000

  Output Delay:- 2500
  Required Time:= 7500
  Launch Clock:- 0
  Input Delay:- 2500
  Data Path:- 1757
  Slack:= 3243
  
```

Cell-Area	Net-Area	Total-Area
542.203	0.000	542.203

< CSLA >

```

Path 1: MET (3694 ps) Late Ext
  Group: clk
  Startpoint: (R) b[1]
  Clock: (R) clk
  Endpoint: (F) cout
  Clock: (R) clk

  Capture
  Clock Edge:+ 10000
  Drv Adjust:+ 0
  Src Latency:+ 0
  Net Latency:+ 0 (
  Arrival:= 10000

  Output Delay:- 2500
  Required Time:= 7500
  Launch Clock:- 0
  Input Delay:- 2500
  Data Path:- 1306
  Slack:= 3694
  
```

Cell-Area	Net-Area	Total-Area
728.482	0.000	728.482

< KSA >

```

Path 1: MET (3789 ps) Late Ext
  Group: clk
  Startpoint: (R) b[4]
  Clock: (R) clk
  Endpoint: (R) sum[7]
  Clock: (R) clk

  Capture
  Clock Edge:+ 10000
  Drv Adjust:+ 0
  Src Latency:+ 0
  Net Latency:+ 0 (
  Arrival:= 10000

  Output Delay:- 2500
  Required Time:= 7500
  Launch Clock:- 0
  Input Delay:- 2500
  Data Path:- 1211
  Slack:= 3789
  
```

Cell-Area	Net-Area	Total-Area
695.218	0.000	695.218

Path




RCA > CSLA > KSA

Area

CSLA > KSA > RCA

그렇다면, 무조건 빠른 회로만 필요할까요?

Propagation delay & Timing

 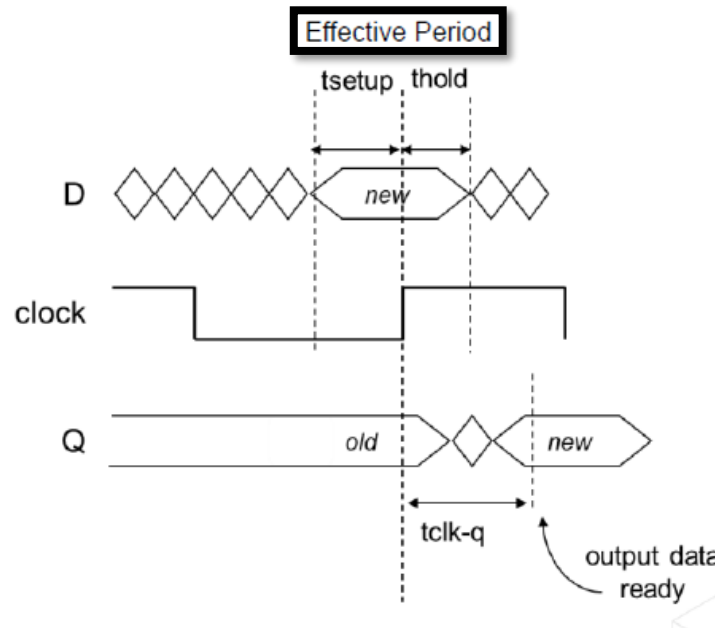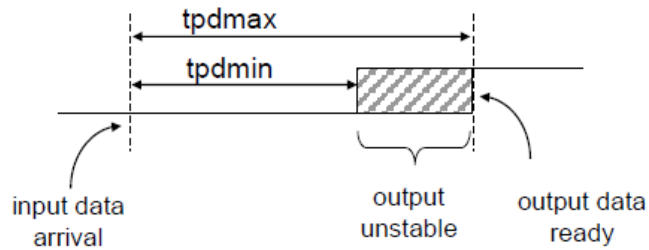


- 가장 짧은 경로 $tpdmin$
- 가장 긴 경로 $tpdmax$

- Edge부터 Data 지연 t_{clk-q}
- Clock 기준으로 setup 전에 준비, hold 까지 유지 되어야 한다

- Clock tree에서 tpd , tsk 파라미터를 고려
- Positive skew는 hold time에, Negative skew는 setup time에 영향

Is delay always a bad thing?

 

Rising edge clock propagation delay at A = $2 + 1.1 + 1.0 = 4.1\text{ns}$

Rising edge clock propagation delay at B = $2 + 1.1 + 1.6 = 4.7\text{ns}$

Clock skew at B with respect to A = $+0.6\text{ns}$ (Positive Skew)

Effective clock period = $20 + 0.6 = 20.6\text{ns}$

Second Clock of B arrives at 24.7ns ($4.7 + 20$)

But, must arrive at 24.5ns because of Setup time.

Data released time from A = $4.1 + 0.5 = 4.6\text{ns}$

Maximum delay = $24.5 - 4.6 = 19.9\text{ns}$

First Clock of B hold time = $4.7 + 0.1 = 4.8\text{ns}$


Data released time from A cannot arrive at B 4.8ns

Minimum delay = $4.8 - 4.6 = 0.2\text{ns}$

반드시 A,B 사이에 Logic 필요

Functional Design Challenges

X-Optimism Simulation Solution

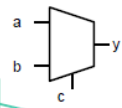

```
// RTL
if ( c )
  y = a; // true
else
  y = b; // other
```

Known as X-Pessimism

Known as X-Optimism

Default

If the condition is unknown, assign the result as stated.

Only FOX guarantees that the simulation has no new unknowns.

```
// Default
a b c : y
0 0 x : 0
0 1 x : 1
1 0 x : 0
1 1 x : 1
```

Forward-Only-X (FOX)

If the condition is unknown, assign the result unknown.

```
// FOX
a b c : y
0 0 x : x
0 1 x : x
1 0 x : x
1 1 x : x
```

Compute-As-Ternary (CAT)



If the condition is unknown, assign the result as the hardware would.

```
// CAT
a b c : y
0 0 x : 0
0 1 x : x
1 0 x : x
1 1 x : 1
```

229 © Cadence Design Systems, Inc. All rights reserved.

cadence

Divergence of CDC Signal

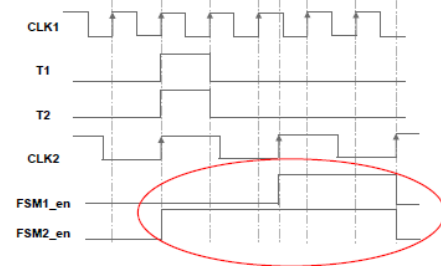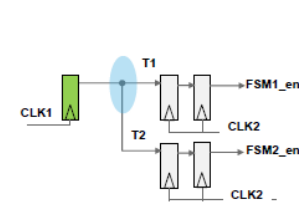

- A divergent logic style to multiple synchronization paths runs the risk of causing functional errors.
- Due to the propagation delay and different metastable settling times, the FSM1_en and FSM2_en could start at different times.
- This type of structure should be avoided by fanning out a single FSM enabled after synchronization to both FSMs.

242 © Cadence Design Systems, Inc. All rights reserved.


cadence

What Is Clock Gating?

A technique used in synchronous circuits to reduce dynamic power by removing the clock when it is not essential to design intent functionality.

- Effectively, we prune the clock tree to save power.
- However, remember the PPA tradeoff?
- This is at the expense of more gates.

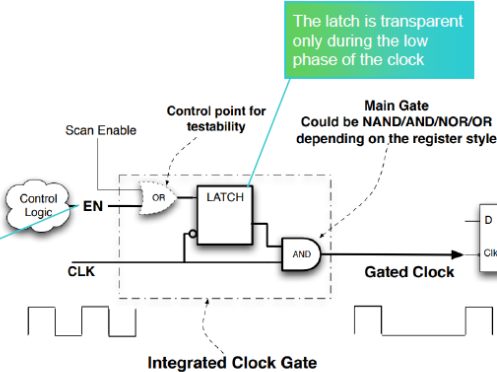
Design Block Enable Signal generated from our Control Logic



256 © Cadence Design Systems, Inc. All rights reserved.

cadence

Power Reduction Technique	Leakage Power	Dynamic Power	Timing	Area Penalty	Methodology Impact	Methodology Change
Low-Power Optimization	10%	10%	0%	10%	None	None
Multi-Vt	6X	0%	0%	0%	Low	Multi-Vt library needed
Clock Gating	0%	20%	0%	<2%	Low	Clock-gating cells needed and extra overhead in STA
Multi-Supply Voltage (MSV)	2X	40-50%	0%	<10%	Medium	Micro-architecture and methodology needs to be domain aware; need voltage regulators and level shifters; verification and analysis challenge
Power Shut-Off (PSO)	10-50X	0%	4-8%	5-15%	Medium-High	Insertion of switch cells; retention flops; wake-up and shut-down time analysis; power shut off and restore verification
Dynamic Voltage Frequency Scaling (DVFS)	2-3X	40-70%	0%	<10%	High	Deterministic scheduling; multi-mode optimization and analysis flow needed; clock synchronization
Substrate Biasing	10X	0%	10%	<10%	High	Maintain well separation; multiple power rail distribution; static timing analysis

 

Thank you.

조남현 선임연구원

EDA | IC

Tel. 010-3219-3897 | **E-mail.** nhcho@npit.co.kr

Web. www.npit.co.kr



